

CSE 260M - Homework 2

Always show all work for full credit.

1. Review: Fill in the missing values in the following table (all values are unsigned)

Binary	Decimal	Hex
1010101		
		0x14A
	238	

2. Write a Boolean equation in sum-of-products canonical form for:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

3. Write a Boolean equation in sum-of-products canonical form for:

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

CSE 260M - Homework 2

4. Write a Boolean equation in sum-of-products canonical form for:

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

5. Write a Boolean equation in sum-of-products canonical form for:

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

CSE 260M - Homework 2

6. Implement the below with only NAND gates (it's the same function in 3). Sketch the circuit (Or use JLS to create the circuit diagram)

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

7. Write the Boolean equation for the circuit below (no need to minimize: give the exact equation implemented in the circuit):

